

(一)

## Design Specification

(1) input & output

main module:

```
input clk,rst; //global clk,rst
output [3:0] q; //作為 led 的輸出
wire clk_d; // F divider 產生的 clk
```


module fd:

```
input clk;
input rst;
output reg clk_out; // output
reg s;           // if(q == 50m) s = 1 else s = 0
reg [26:0]q;     // 計數
```

module counter:

```
input clk;
input rst;
output reg [3:0]out;
```

(2) block diagram

 

```

input clk;
input rst;
output [3:0]b;
wire clk_d;

fd U0(.clk(clk), .rst(rst), .clk_out(clk_d));
counter U1(.clk(clk_d), .rst(rst), .out(b));

```

## Design Implementation

### (1) I/O PIN

```

set_property PACKAGE_PIN V19 [get_ports {b[3]}]
set_property PACKAGE_PIN U19 [get_ports {b[2]}]
set_property PACKAGE_PIN E19 [get_ports {b[1]}]
set_property PACKAGE_PIN U16 [get_ports {b[0]}]
set_property PACKAGE_PIN W5 [get_ports clk]
set_property PACKAGE_PIN V17 [get_ports rst]

```

### (2) verilog code

```

module fd(clk, rst, clk_out);
    input clk;
    input rst;
    output reg clk_out;
    reg s;
    reg [26:0]q;


    always@(posedge clk or negedge rst)
        if (~rst || s == 1) q <= 0;
        else q <= q + 1;

    always @*
        if (q == 27'd50000000) s = 1;
        else s = 0;

    always@(posedge clk or negedge rst)
        if (~rst) clk_out <= 0;
        else clk_out <= clk_out ^ s;

endmodule

```

 

```
module counter(clk, rst, out);
```

```
    input clk;
```

```
    input rst;
```


```
    output reg [3:0]out;
```

```
    always@(posedge clk or negedge rst)
```

```
        if (~rst) out <= 0;
```

```
        else out = out + 1;
```

```
endmodule
```

 

## DISCUSSION

這次的想法很簡單，就只是 1 個 f divider 接一個 counter，基本上把以前打過的 module 接一接就完成了。實驗結果就是 4 個 led 燈個當 b 的 4 個 bit，然後每秒都會看到 led 燈 output 的結果+1。

## CONCLUSION

這個 lab 讓我對模組之間的連接更熟悉

(二)

### Design Specification

(1)


```
module main(clk, rst, light, ssd);  
  input clk;  
  input rst;  
  output [3:0]light; // light of seven segment display  
  output [7:0]ssd; // seven segment display  
  wire [3:0]value; // the counting number  
  wire clk_d; // clock generated by f divider
```

```
module fd(clk, rst, clk_out);  
  reg [26:0]q;  
  input clk;  
  input rst;  
  output clk_out;
```

```
module BCD_UP(clk, rst, q);  
  input clk;  
  input rst;  
  output reg [3:0]q;  
  reg [3:0]q_temp;
```

```
module DEC(in, out);  
  input [3:0]in;  
  output reg [7:0]out;
```

(2) Block diagram

 

```
fd U0(.clk(clk), .rst(rst), .clk_out(clk_d));
BCD_UP U1(.clk(clk_d), .rst(rst), .q(value));
DEC U2(.in(value), .out(ssd));
assign light = 4'b1110;
```


DESIGN IMPLEMENTATION

(1) I/O PINS

```
set_property PACKAGE_PIN W4 [get_ports {light[3]}]
set_property PACKAGE_PIN V4 [get_ports {light[2]}]
set_property PACKAGE_PIN U4 [get_ports {light[1]}]
set_property PACKAGE_PIN U2 [get_ports {light[0]}]
set_property PACKAGE_PIN W7 [get_ports {ssd[7]}]
set_property PACKAGE_PIN W6 [get_ports {ssd[6]}]
set_property PACKAGE_PIN U8 [get_ports {ssd[5]}]
set_property PACKAGE_PIN V8 [get_ports {ssd[4]}]
set_property PACKAGE_PIN U5 [get_ports {ssd[3]}]
set_property PACKAGE_PIN V5 [get_ports {ssd[2]}]
set_property PACKAGE_PIN U7 [get_ports {ssd[1]}]
set_property PACKAGE_PIN V7 [get_ports {ssd[0]}]
set_property PACKAGE_PIN W5 [get_ports clk]
set_property PACKAGE_PIN V17 [get_ports rst]
```
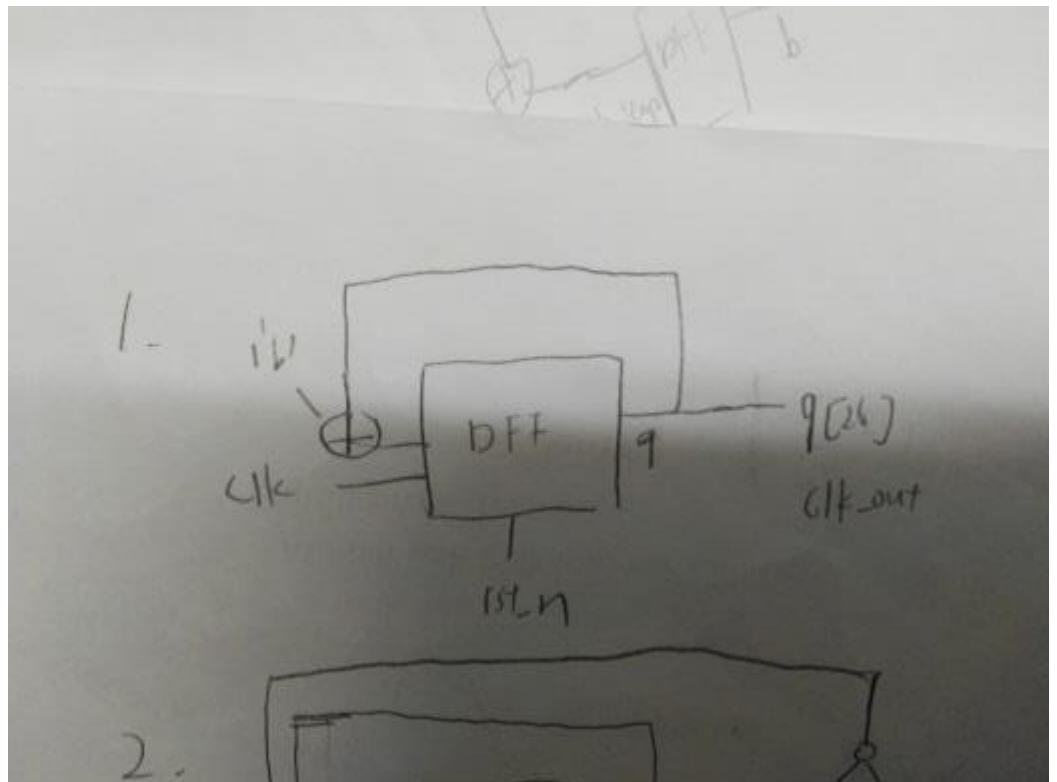
## (2) Verilog code

```
module fd(clk, rst, clk_out);  
    reg [26:0]q;  
    input clk;  
    input rst;  
    output clk_out;  
  
    always @(posedge clk or negedge rst)  
        if (~rst) q <= 0;  
        else q <= q + 1'b1;  
  
    assign clk_out = q[26];  
  
endmodule
```



```


module BCD_UP(clk, rst, q);
    input clk;
    input rst;
    output reg [3:0] q;
    reg [3:0] q_temp;

    always @*
        if (q == 4'b1001) q_temp = 4'b0000;
        else q_temp = q + 1'b1;

    always @(posedge clk or negedge rst)
        if (~rst) q <= 4'b0000;
        else q <= q_temp;

endmodule

```

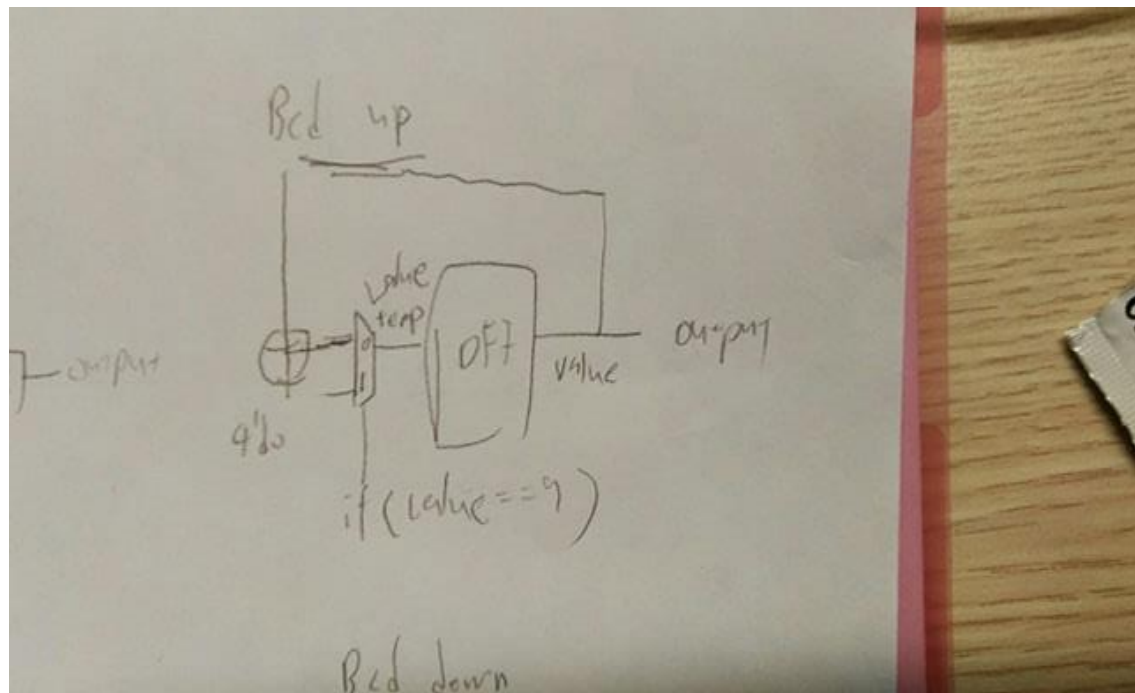


```

module DEC(in, out);
    input [3:0]in;
    output reg [7:0]out;

    always @*
        case(in)
            4'd0: out = `SS_0;
            4'd1: out = `SS_1;
            4'd2: out = `SS_2;
            4'd3: out = `SS_3;
            4'd4: out = `SS_4;
            4'd5: out = `SS_5;
            4'd6: out = `SS_6;
            4'd7: out = `SS_7;
            4'd8: out = `SS_8;
            4'd9: out = `SS_9;
            default: out = 8'b11111111;
        endcase
endmodule

```

 

#### DISCUSSION

這題的想法其實不難，因為我們已經做過 1HZ 的 f divider，跟這題十分相似，只是我 bcd\_up module 那裏忘記宣告成 3-bit，導致我跳出來只有 0 跟 1。

Output 的結果就是從 0 數到 9 再跳回 0。

#### CONCLUSION

這題讓我對 VERILOG 更熟悉



(三)

### Design Specification

```
module main(clk, rst, light, ssd);
```

```
    input clk;
```

```
    input rst;
```

```
    output [3:0]light;
```

```
    output [7:0]ssd;
```

```
    wire [3:0]value;
```

```
    wire clk_d;
```

```
module BCD_DOWN(clk, rst, q);
```

```
    input clk;
```

```
    input rst;
```

```
    output reg [3:0]q;
```


```
    reg [3:0]q_temp;
```

```
module DEC(in, out);    // decorder
```

```
    input [3:0]in;
```

```
    output reg [7:0]out;
```

block diagram:

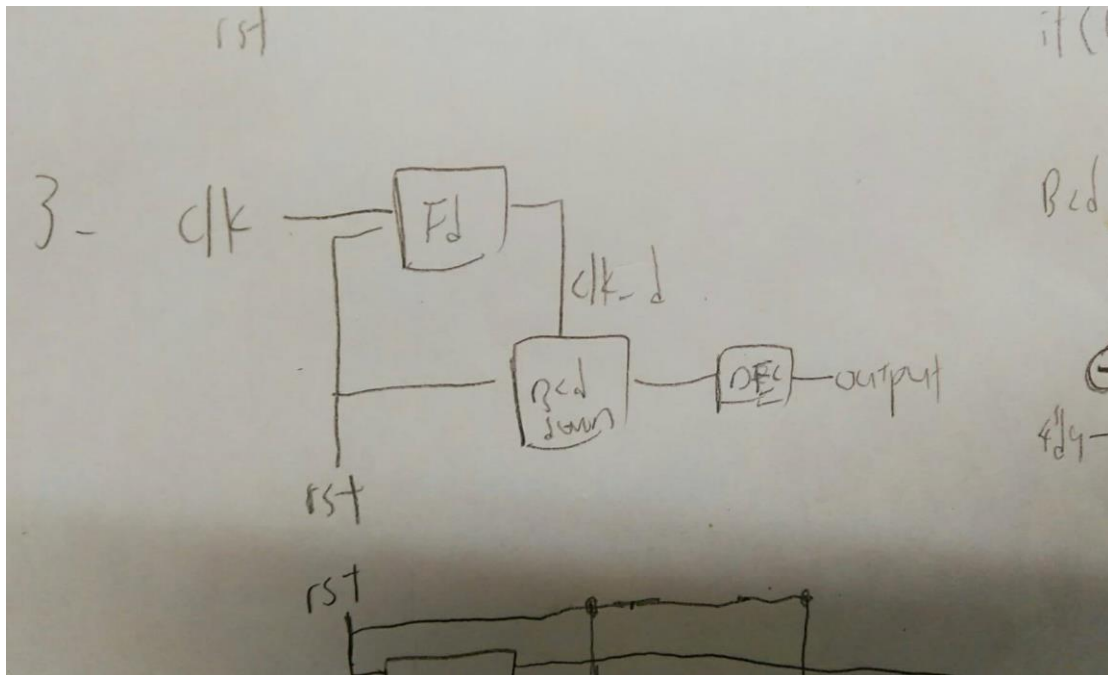

```

fd U0(.clk(clk), .rst(rst), .clk_out(clk_d));
BCD_DOWN U1(.clk(clk_d), .rst(rst), .q(value));
DEC U2(.in(value), .out(ssd));
assign light = 4'b1110;

```

## DESIGN IMPLEMENTATION

### (1) I / O PINS

```


set_property PACKAGE_PIN W4 [get_ports {light[3]}]
set_property PACKAGE_PIN V4 [get_ports {light[2]}]
set_property PACKAGE_PIN U4 [get_ports {light[1]}]
set_property PACKAGE_PIN U2 [get_ports {light[0]}]
set_property PACKAGE_PIN W7 [get_ports {ssd[7]}]
set_property PACKAGE_PIN W6 [get_ports {ssd[6]}]
set_property PACKAGE_PIN U8 [get_ports {ssd[5]}]
set_property PACKAGE_PIN V8 [get_ports {ssd[4]}]
set_property PACKAGE_PIN U5 [get_ports {ssd[3]}]
set_property PACKAGE_PIN V5 [get_ports {ssd[2]}]
set_property PACKAGE_PIN U7 [get_ports {ssd[1]}]
set_property PACKAGE_PIN V7 [get_ports {ssd[0]}]
set_property PACKAGE_PIN W5 [get_ports clk]
set_property PACKAGE_PIN V17 [get_ports rst]

```

### (2) CODE

Code is same as 4-2

Only bcd\_down is different

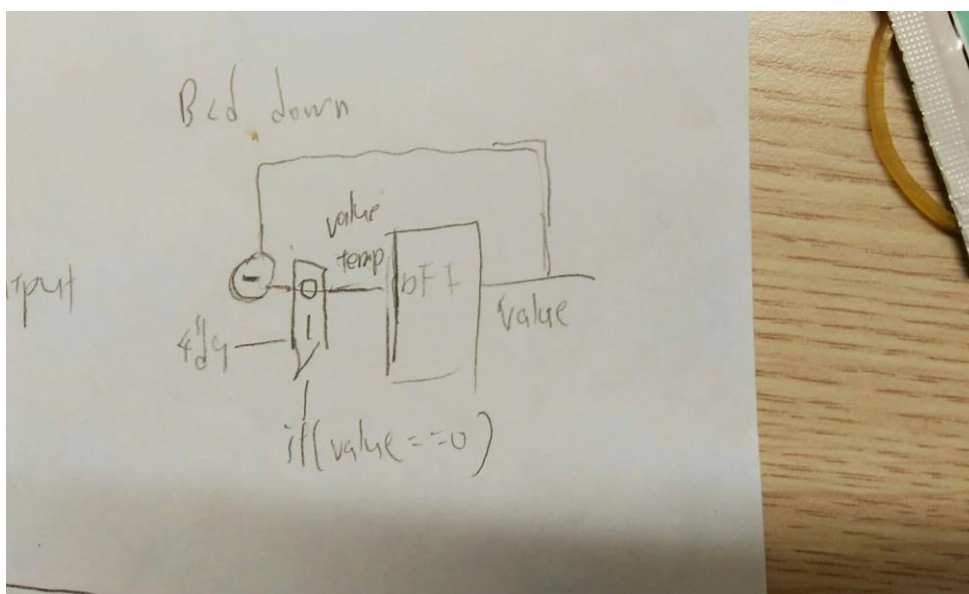

```

module BCD_DOWN(clk, rst, q);
    input clk;
    input rst;
    output reg [3:0]q;
    reg [3:0]q_temp;

    always @*
        if (q == 4'b0000) q_temp = 4'b1001;
        else q_temp = q - 1'b1;

    always @(posedge clk or negedge rst)
        if (~rst) q <= 4'b0000;
        else q <= q_temp;

endmodule

```

### Discussion

這題跟第 2 提根本一樣，我是直接複製貼上，再把 bcd\_down 裡面+改成減，然後數到 0 時，重製成 9

結果就是從 9 數到 0 再跑回 9 重數

### (四)

### Design Specification

```

module main(clk, rst, light, ssd);
    input clk;
    input rst;
    output [3:0]light;
    output [7:0]ssd;

    wire enable; // count enable
    wire [3:0]value0; // 個位
    wire [3:0]value1; // 十位
    wire clk_d; // clock of fd
    wire clk_scan; // clock of scan control
    wire [1:0]borrow; // 借位
    wire [3:0]num; // 要 input 到 decorder 的數字

```

```

module FD(clk, rst, clk_out, clk_out2);
    input clk;
    input rst;
    output reg clk_out ;    // clock for fd
    output clk_out2;        // clock for scan control
    reg s;

    reg [26:0]Q;            // 記數
    reg [26:0]Q_temp;

```

```

module BCD_DOWN(limit, clk, rst, decrease, q, borrow);
    input [3:0]limit;    // 初始值
    input clk;
    input rst;
    input decrease;    // 判斷要不要減
    output reg [3:0]q;    // output 值
    output reg borrow;    // 判斷要不要借位
    reg [3:0]q_temp;

```

```

module SCAN(control, rst, in0, in1, light, out);
    input control;
    input rst;
    input [3:0]in0;
    input [3:0]in1;
    output reg [3:0]light;
    output reg [3:0]out;

```

```

module DEC(in, out);
    input [3:0]in;
    output reg [7:0]out;


```

```

module STOP(in1, in2, out);
    input [3:0]in1;    // 個位
    input [3:0]in2;    // 十位
    output reg out;

```

block diagram

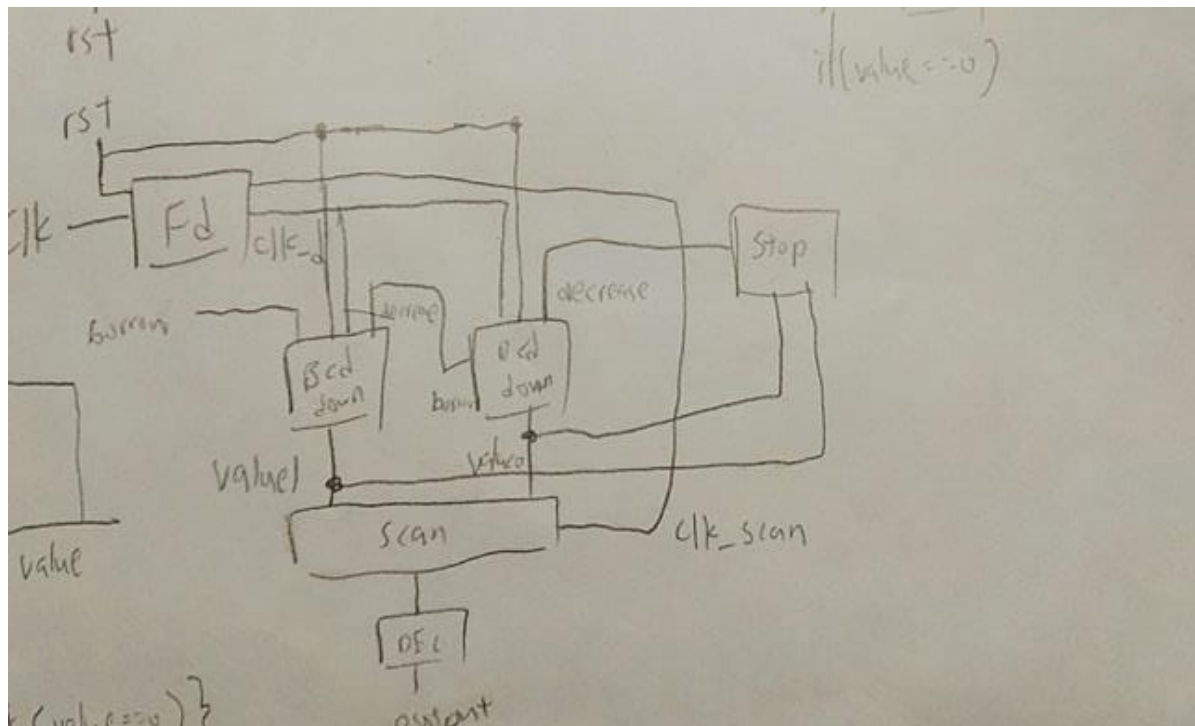

```

FD U0(.clk(clk), .rst(rst), .clk_out(clk_d), .clk_out2(clk_scan));
STOP U3(.in1(value1), .in2(value0), .out(enable));
BCD_DOWN digit1(.limit(4'b0000), .clk(clk_d), .rst(rst), .decrease(enable), .q(value0), .borrow(borrow[0]));
BCD_DOWN digit2(.limit(4'b0011), .clk(clk_d), .rst(rst), .decrease(borrow[0]), .q(value1), .borrow(borrow[1]));
SCAN U1(.control(clk_scan), .rst(rst), .in0(value0), .in1(value1), .light(light), .out(num));
DEC U2(.in(num), .out(ssd));

```

module

## Design implementation

### (1) I / O PINS

```

set_property PACKAGE_PIN W4 [get_ports {light[3]}]
set_property PACKAGE_PIN V4 [get_ports {light[2]}]
set_property PACKAGE_PIN U4 [get_ports {light[1]}]
set_property PACKAGE_PIN U2 [get_ports {light[0]}]
set_property PACKAGE_PIN W7 [get_ports {ssd[7]}]
set_property PACKAGE_PIN W6 [get_ports {ssd[6]}]
set_property PACKAGE_PIN U8 [get_ports {ssd[5]}]
set_property PACKAGE_PIN V8 [get_ports {ssd[4]}]
set_property PACKAGE_PIN U5 [get_ports {ssd[3]}]
set_property PACKAGE_PIN V5 [get_ports {ssd[2]}]
set_property PACKAGE_PIN U7 [get_ports {ssd[1]}]
set_property PACKAGE_PIN V7 [get_ports {ssd[0]}]

```

```
set_property PACKAGE_PIN W5 [get_ports clk]
set_property PACKAGE_PIN V17 [get_ports rst]
```

## (2) CODE

```
module FD(clk, rst, clk_out, clk_out2);
    input clk;
    input rst;
    output reg clk_out = 0;
    output clk_out2;
    reg s;



    reg [26:0]Q;
    reg [26:0]Q_temp;

    always @*
        Q_temp = Q + 1'b1;
    always @(posedge clk or negedge rst)
        if (~rst || s == 1) Q <= 27'd0;
        else Q <= Q_temp;


    always @(posedge clk or negedge rst)
        if (~rst)
            clk_out <= 0;
        else
            clk_out <= clk_out ^ s;

      always @*
        if (Q == 27'd50000000 - 1) begin
            s = 1;
        end
        else begin
            s = 0;
        end
    assign clk_out2 = Q[14];
endmodule
```





 *borrow* signal in low the *decrease* control






```

module SCAN(control, rst, in0, in1, light, out);
    input control;
    input rst;
    input [3:0]in0;
    input [3:0]in1;
    output reg [3:0]light;
    output reg [3:0]out;

    always @*
        if (control == 1'b0) begin
            light = 4'b1110;
            out = in0;
        end
        else begin
            light = 4'b1101;
            out = in1;
        end
    end
endmodule

```

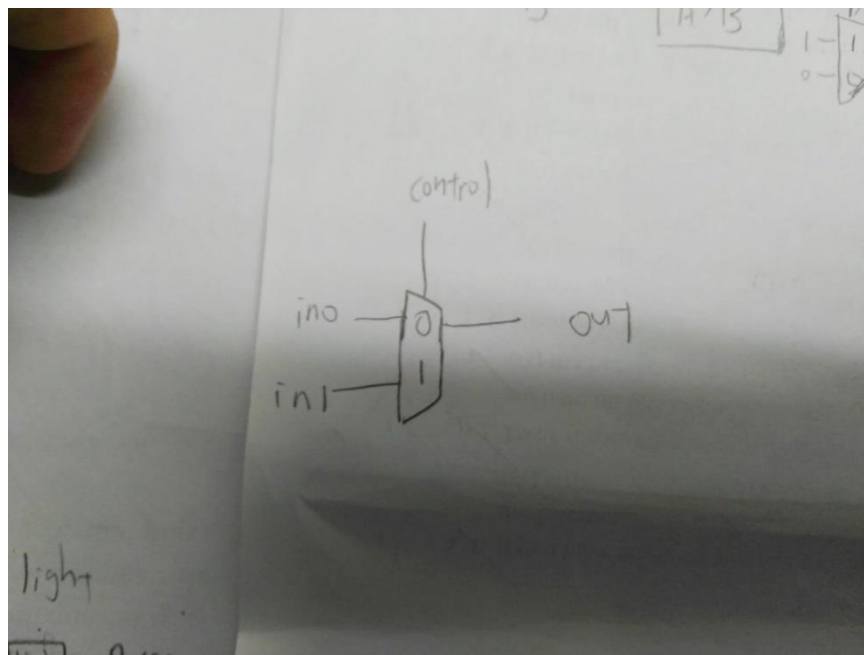


```

module DEC(in, out);
    input [3:0]in;
    output reg [7:0]out;

    always @*
        case(in)
            4'd0: out = `SS_0;
            4'd1: out = `SS_1;
            4'd2: out = `SS_2;
            4'd3: out = `SS_3;
            4'd4: out = `SS_4;
            4'd5: out = `SS_5;
            4'd6: out = `SS_6;
            4'd7: out = `SS_7;
            4'd8: out = `SS_8;
            4'd9: out = `SS_9;
            default: out = 8'b11111111;
        endcase
endmodule

```

 

```

module STOP(in1, in2, out);
    input [3:0]in1;
    input [3:0]in2;
    output reg out;

    always @*
        if (in1 == 4'b0000 && in2 == 4'b0000) out = 0;
        else out = 1;
endmodule

```

### discussion

這題複雜很多，`down_counter` 需要多加一個 `borrow` 跟 `decrease`，分別是下一位要不要減跟這一位要不要減，還要用 `scancontrol` 去顯示 2 個不同的數字，最後還寫了一個 `stopmodule` 去停在 00。

這題遇到跟以前一樣的問題，就是只會顯示 1 跟 0，但由於前面犯過了錯，我馬上去檢查哪裡少宣告成 4-bit，結果就解決了。

結果就是從 30 數到 00 然後停住。

### Conclusion

這題其實花我很久，我聽完老師講之後，架構很快就打完了，可是 `debug` 找了很久，因為有太多地方要宣告成 4bit，導致我找到幾個後以為沒錯了，轉而去檢查其他對的地方。