

LAB02

1.

Design specification

output cout, s;


input x, y, cin;

$\text{cout} = xy \mid x\text{cin} \mid y\text{cin};$

$s = x \oplus y \oplus \text{cin}$

Design implementation

diagram

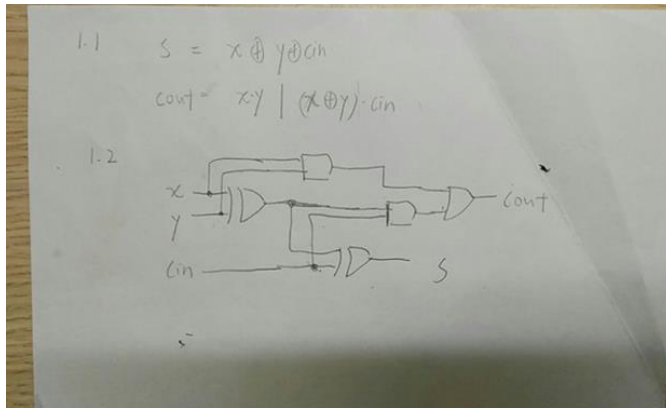

assign cout = x & y | x & cin | y & cin;

assign s = x ^ y ^ cin;

I/O PINS

set_property PACKAGE_PIN U16 [get_ports cout]

set_property PACKAGE_PIN E19 [get_ports s]

set_property PACKAGE_PIN W16 [get_ports cin]

set_property PACKAGE_PIN V17 [get_ports x]

set_property PACKAGE_PIN V16 [get_ports y]

Discussion:

其實老師上完還對板子一無所知，我問同學才知道要用板子當 testbench，那個開關是控制 input 的，還有 input 的腳位在開關下方

Conclusion


第一次完板子，覺得很酷

2.

Design specification:

```
input [3:0]i;
output [7:0]D_ssd;      // seven segment display
output [3:0]light;      // light of seven segment display
output [3:0]d;          // led
light = 4'b0000;
d = i;
```

Diagram

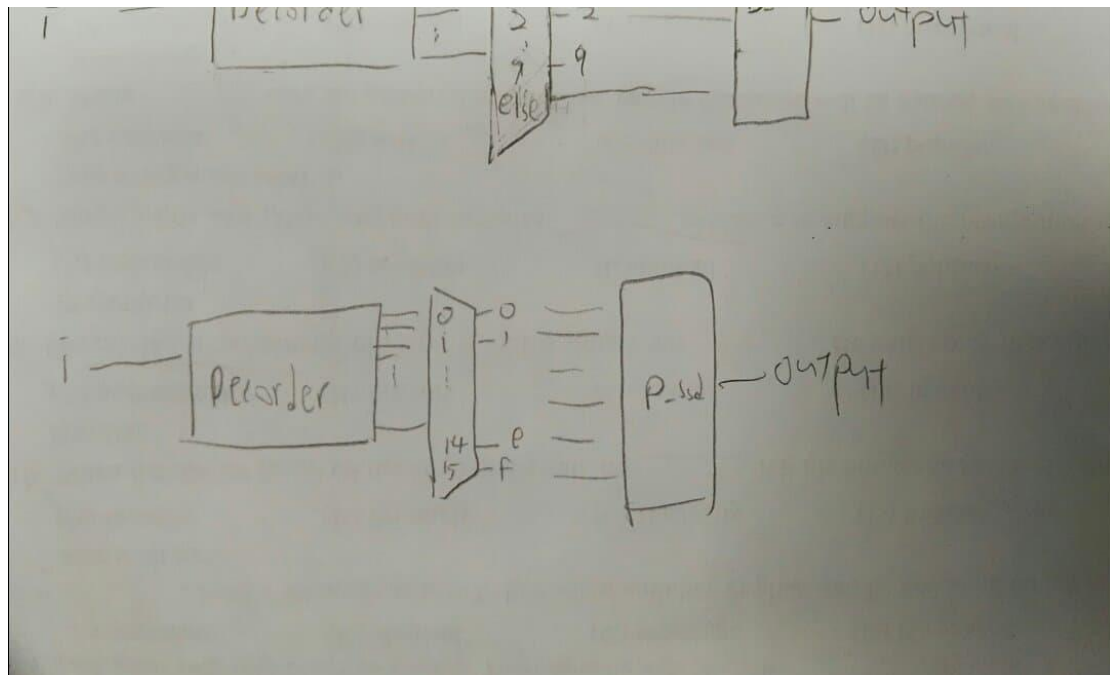

Design implementation

```
display U0(i, D_ssd);
```

```
assign light = 4'b0000;
assign d = i;
```

```
`define SS_0 8'b00000011
`define SS_1 8'b10011111
`define SS_2 8'b00100101
`define SS_3 8'b00001101
`define SS_4 8'b10011001
`define SS_5 8'b01001001
```

```
`define SS_6 8'b01000001
`define SS_7 8'b00011111
`define SS_8 8'b00000001
`define SS_9 8'b00001001
```

```
module display(in, segs);
    input [3:0]in;
    output reg [7:0]segs;

    always @*
        case (in)
            4'd0: segs = `SS_0;
            4'd1: segs = `SS_1;
            4'd2: segs = `SS_2;
            4'd3: segs = `SS_3;
            4'd4: segs = `SS_4;
            4'd5: segs = `SS_5;
            4'd6: segs = `SS_6;
            4'd7: segs = `SS_7;
            4'd8: segs = `SS_8;
            4'd9: segs = `SS_9;
            default: segs = 8'b01110001;
        endcase
endmodule
```

I/O PINS

```
set_property PACKAGE_PIN V19 [get_ports {d[3]}]
set_property PACKAGE_PIN U19 [get_ports {d[2]}]
set_property PACKAGE_PIN E19 [get_ports {d[1]}]
set_property PACKAGE_PIN U16 [get_ports {d[0]}]
set_property PACKAGE_PIN W7 [get_ports {D_ssd[7]}]
set_property PACKAGE_PIN W6 [get_ports {D_ssd[6]}]
set_property PACKAGE_PIN U8 [get_ports {D_ssd[5]}]
set_property PACKAGE_PIN V8 [get_ports {D_ssd[4]}]
set_property PACKAGE_PIN U5 [get_ports {D_ssd[3]}]
set_property PACKAGE_PIN V5 [get_ports {D_ssd[2]}]
set_property PACKAGE_PIN U7 [get_ports {D_ssd[1]}]
set_property PACKAGE_PIN V7 [get_ports {D_ssd[0]}]
```

```
set_property IOSTANDARD LVCMOS33 [get_ports {i[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {i[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {i[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {i[0]}]
set_property PACKAGE_PIN W4 [get_ports {light[3]}]
set_property PACKAGE_PIN V4 [get_ports {light[2]}]
set_property PACKAGE_PIN U4 [get_ports {light[1]}]
set_property PACKAGE_PIN U2 [get_ports {light[0]}]
```

Discussion:

這次沒遇到沒什麼問題，唯一的就引用另一個 module 時，我沒有給他一個名子，我原本寫 `display (i, D_ssd);` 然後有錯，才改成 `display U0(i, D_ssd);`

Conclusion:

這次感覺很新奇，居然可以讓燈亮，希望以後能讓 4 個燈亮不同的字。

3.

Design specification

```
input [3:0]i;
```


```
output [7:0]D;
```

```
output [3:0]d;
```

```
output [3:0]light;
```

```
light = 4'b0000;
```

```
d = i;
```

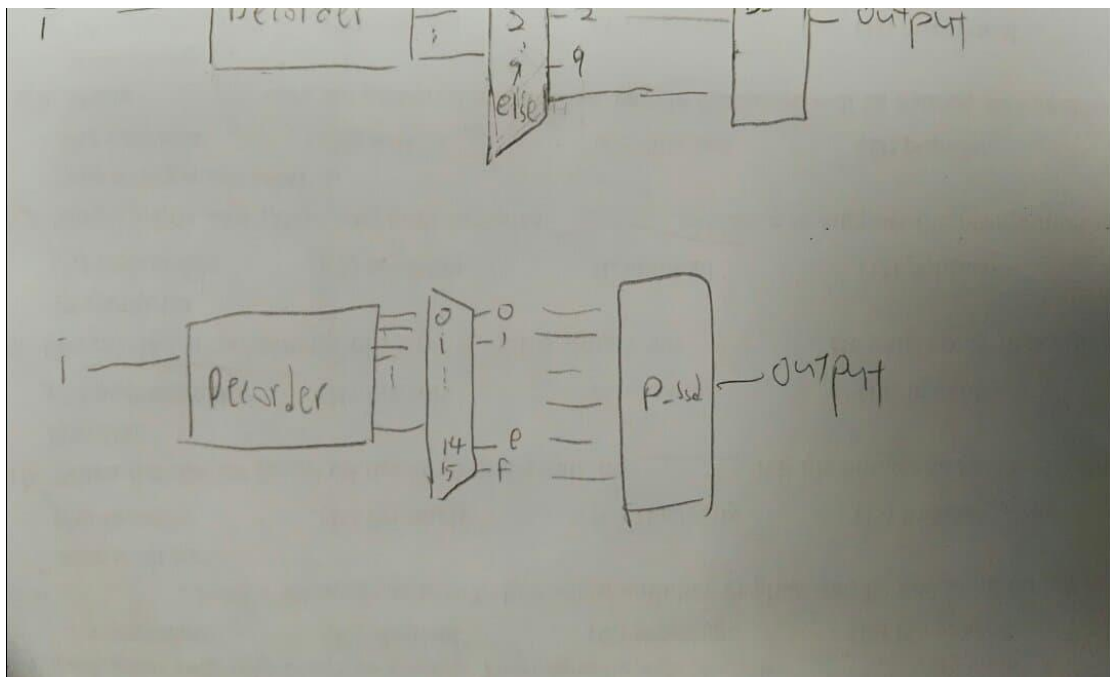

Design implementation

```
display U0(i, D);
```

```
assign light = 4'b0000;
```

```
assign d = i;
```

```
`define SS_0 8'b00000011
```

```
`define SS_1 8'b10011111
```

```
`define SS_2 8'b00100101
```

```
`define SS_3 8'b00001101
```

```
`define SS_4 8'b10011001
```

```
`define SS_5 8'b01001001
```

```

`define SS_6 8'b01000001
`define SS_7 8'b00011111
`define SS_8 8'b00000001
`define SS_9 8'b00001001
`define SS_10 8'b00010001
`define SS_11 8'b11000001
`define SS_12 8'b11100101
`define SS_13 8'b10000101
`define SS_14 8'b01100001
`define SS_15 8'b01110001

```

```

module display(in, DEC);
    input [3:0]in;
    output reg [7:0]DEC;
    always @*
    case (in)
        4'd0: DEC = `SS_0;           // decoder
        4'd1: DEC = `SS_1;
        4'd2: DEC = `SS_2;
        4'd3: DEC = `SS_3;
        4'd4: DEC = `SS_4;
        4'd5: DEC = `SS_5;
        4'd6: DEC = `SS_6;
        4'd7: DEC = `SS_7;
        4'd8: DEC = `SS_8;
        4'd9: DEC = `SS_9;
        4'd10: DEC = `SS_10;
        4'd11: DEC = `SS_11;
        4'd12: DEC = `SS_12;
        4'd13: DEC = `SS_13;
        4'd14: DEC = `SS_14;
        4'd15: DEC = `SS_15;
        default: DEC = 8'b11111111;
    endcase
endmodule

```

Discussion:

這題跟第二題差不多，在多加幾個 output 型式就好

4.

Design specification

input [3:0]A, B;

output reg X;

output [3:0]a;


output [3:0]b;

a = A;

b = B;

if (A > B) x = 1;

else x = 0;

 

Design implementation

```
always @* begin
```

```
    if (A > B) X = 1;
```

```
    else X = 0;
```

```
end
```

```
assign a = A;
```

```
assign b = B;
```

discussion

這次的想法引簡單，如果 $a > b$ 就 output 1，否則 output 0;

Conclusion

這次本來以為會很難，因為以前畫比較器很複雜，但他有大於這個功能真的很方便，減少了一大堆線路。