

Verilog HDL (2)

Hsi-Pin Ma

<http://lms.nthu.edu.tw/course/38127>

Department of Electrical Engineering
National Tsing Hua University

Lexical Conventions

White Space and Comments


- White space makes code more readable
 - Include blank space (`\b`), tabs (`\t`), and carriage return (`\n`).
- Comments
 - `/* ... */` : mark more than one line
 - `//` : mark only one line.

Identifiers

- Identifiers are user-provided names for Verilog objects within a description.
- Legal characters in identifiers:
 - a-z, A-Z, 0-9, _, \$
- The first character of an identifier must be an alphabetical character (a-z, A-Z) or an underscore (_).
- Identifiers can be up to 1023 characters long.

Identifiers

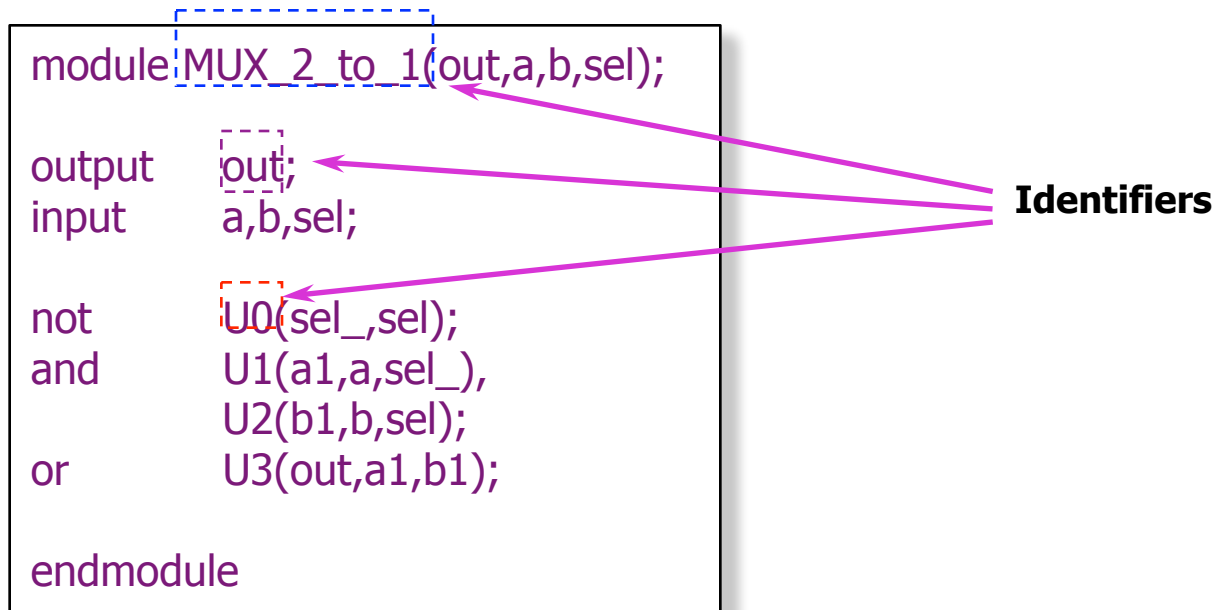- Names of modules, ports, and instances are identifiers.



Keywords





- Pre-defined non-escaped identifiers that used to define the language construct.
- All keywords are defined in lower cases.
- Examples
 - module, endmodule
 - input, output, inout
 - reg, integer, real, time
 - not, and, or, nand, nor, xor
 - parameter
 - begin, end
 - fork, join
 - always, for
 - ...

Case Sensitivity

- Verilog is a case sensitive language.
- Use “-u” option in command line option for case-insensitive.

Value Sets

- 4-value logic system in Verilog

    

Integer and Real Numbers

- Numbers can be integer or real numbers.
- Integer can be sized or unsized. Sized integer can be represented as
 - `<size>'<base><value>`
 - size : size in bits
 - base : can be b(binary), o(octal), d(decimal), or h(hexadecimal)
 - value : any legal number in the selected base and x, z, ?.
- Real numbers can be represented in decimal or scientific format.

Integer and Real Numbers

- 16 : 32 bits decimal
- 8'd16
- 8'h10
- 8'b0001_0000
- 8'o20
- 32'bx : 32 bits x
- 2'b1? : ? represents a high impedance bit
- 6.3
- 5.3e-4
- 6.2e3

Concatenation and Replication Operators


- Bit replication for 01010101
 - assign byte = {4{2'b01}};
- Sign extension
 - assign word = {{8{byte[7]}},byte};

Major Data Type Class

- Nets
 - Physical connection between devices
- Registers
 - Represent abstract storage elements
- Parameters
 - Configure module instances

Nets

 - Physical connections between structural entities.
- Must be driven by a driver, such as a **gate instantiation** or **continuous assignment**
- As the driver changes its value, Verilog automatic propagates the value onto a net.
- Default value is **z** if no drivers are connected to net



Registers

- Registers represent **abstract** storage elements.
- A register holds its value until a new value is assigned to it.
- Registers are used extensively in behavior modeling and in applying stimuli.
- Default value is X.

Type of Registers


- **reg**
 - Unsigned integer variable of varying bit width
- **integer**
 - Signed integer variable, 32-bit wide. Arithmetic operations produce 2's complement results.
- **real**
 - Signed floating point variable, double precision
- **time**
 - Unsigned integer variable, 64-bit wide.
- **Do not confuse register data type with structural storage element (e.g. D-type FF)**

Declaration Syntax of Verilog Registers

- `reg <range> ? <name> <,<name>>*;`
- Example
 - `reg a;`
 - `reg [5:2] b,c;`

Choosing the Correct Data Types

 - An **input** or **inout** port must be a net.
- An **output** port can be a register data type.
- A signal assigned a value in a procedural block must be a register data type.



Common Mistakes in Choosing Data Types

- Make a procedural assignment to a net

```
wire [7:0] databus;
always @(read or addr) databus=read ? mem[addr] : 'bz;
```

Illegal left-hand-side assignment
- Connect a register to an instance output

```
reg myreg;
and (myreg, net1, net2);
```

Illegal output port specification
- Declare a module **input** port as a register

```
input myinput;
reg myinput;
```

Incompatible declaration

Procedural Assignments

```

module assignment_test;
reg [3:0] a,b;
wire [4:0] sum1;
reg [4:0] sum2;

```

```

assign sum1 = a + b ;

```

```

initial
begin

```

```

  a=4'b1010;b=4'b0110;

```

```

  sum2 = a + b;

```

```

  $display("\a b sum1 sum2);

```

```

  $monitor(a,b,sum1,sum2);

```

```

  #10 a=4'b0001;

```

```

end

```

```

endmodule

```

Continuous assignment

Procedural assignment

```

module FA(s,co,a,b,ci);
input a,b,ci;
output s,co;
reg s;

```

```

s=a^b^ci;

```

```

always @*
begin

```

```

  assign co=(a&b)|(b&ci)|
  (a&ci);

```

```

end

```

```

endmodule

```

Error! Illegal left-hand-side
continuous assignment.

Error! Illegal left-hand-side
in assign statement.


Behavior Modeling

At every positive edge of CLOCK

If PRESET and CLEAR are not low
set Q to the value of D

Whenever PRESET goes low
set Q to logic 1

Whenever CLEAR goes low
set Q to logic 0


 


Behavior Modeling

- In behavior modeling, you must specify your circuit's
 - Action
 - How to model the circuit's behavior
 - Timing control
 - Timing
 - Condition
- Verilog supports the following structures for behavior modeling
 - Procedural block
 - Procedural assignment
 - Timing control
 - Control statement

Procedural Blocks

  
- In Verilog, procedural blocks are basis of behavior modeling
- Procedural blocks are of two types
 - initial procedural block, which execute only once
 - always procedural block, which execute in a loop



Procedural Blocks

- All procedural blocks are activated at simulation time 0.
 - The block will not be executed until the enabling condition evaluates TRUE.
 - Without the enabling condition, the block will be executed immediately.

Activated at simulation time 0

 

Statement will not be executed until the condition c is TRUE.


Procedural Blocks

```
module clock_gen(phi1,phi2);  
output    phi1,phi2;  
reg phi1,phi2;
```

```
initial  
begin  
    phi1=0;phi2=0  
end
```

```
always  
    #100 phi1=~phi1;
```
 
```
always    @(posedge phi1)  
begin  
    phi2=1;  
    #50    phi2=0;  
    #50    phi2=1;  
    #50    phi2=0;  
end  
endmodule
```



These procedural blocks are activated and executed at simulation time 0

This procedural block is activated at simulation time 0 but executed at positive edge of phi1

Procedural Blocks


- Three components
 - Procedural assignment statements
 - High-level programming language constructs
 - Timing controls
- Using the first two components to model the actions of the circuit.
- Using timing controls to model when should these actions happen.

Procedural Timing Control


- Three types
 - Simple delay control
 - #50 clk=~clk;
 - Event control
 - @* sum=a+b+ci;
 - @(posedge clk) q<=d;
 - Level-sensitive timing control

Examples

2-bit Absolute Value Calculator (1/2)

 

 - 2 If z is negative (MSB is 1), complement every bit and add 1. If z is positive (MSB is 0), keep all bits the same. Use XOR for MSB and every bit.



2-bit Absolute Value Calculator (2/2)

Module (abs.v)

5

```
module abs(
    z_abs, // absolute value of z
    z // original value
);

output [2:0] z_abs; // absolute value of z
input [1:0] z; // original value

reg [1:0] z_tmp; // XOR output
reg [2:0] z_abs; // register for Z

// Combinational logics:
always @*
begin
    z_tmp[1]=z[1]^z[1];
    z_tmp[0]=z[0]^z[1];
    z_abs={z_tmp[1],z_tmp[0]}+{2'b0,z[1]};
end

endmodule
```

Testbench (t_abs.v)

6

```
module t_abs;

wire [2:0] z_abs; // absolute value of z
reg [1:0] z; // original value

abs U0(.z_abs(z_abs),.z(z));

initial
begin
    z=2'b00;
    #5 z=2'b01;
    #5 z=2'b10;
    #5 z=2'b11;
    #5 z=2'b00;
end

endmodule
```

Binary Up Counter

```

`define CNT_BIT_WIDTH 4
module bincnt(
    q, // output
    clk, // global clock
    rst_n // active low reset
);


output [`CNT_BIT_WIDTH-1:0] q; // output
input clk; // global clock
input rst_n; // active low reset

reg [`CNT_BIT_WIDTH-1:0] q; // output (in always block)
reg [`CNT_BIT_WIDTH-1:0] q_tmp; // input to dff (in always block)

// Combinational logics
always @*
    q_tmp = q + 1'b1;

// Sequential logics: Flip flops
always @(posedge clk or negedge rst_n)
    if (~rst_n) q <= `CNT_BIT_WIDTH'd0;
    else q <= q_tmp;

endmodule
  
```

 

Frequency Divider

```

`define FREQ_DIV_BIT 27
module freqdiv(
  clk_out, // divided clock output
  clk, // global clock input
  rst_n // active low reset
);


output clk_out; // divided output
input clk; // global clock input
input rst_n; // active low reset

reg clk_out; // clk output (in always block)
reg [FREQ_DIV_BIT-2:0] cnt; // remainder of the counter
reg [FREQ_DIV_BIT-1:0] cnt_tmp; // input to dff (in always block)

// Combinational logics: increment, neglecting overflow
always @*
  cnt_tmp = {clk_out,cnt} + 1'b1;

// Sequential logics: Flip flops
always @(posedge clk or negedge rst_n)
  if (~rst_n) {clk_out, cnt} <= `FREQ_DIV_BIT'd0;
  else {clk_out,cnt} <= cnt_tmp;

endmodule
  
```

 

cnt_tmp[26:0]

cnt[26:0]

Frequency Divider

```

`define FREQ_DIV_BIT 27
module freqdiv27(
    clk_out, // divided clock output
    clk_ctl, // divided clock output for scan freq
    clk, // global clock input
    rst_n // active low reset
);

output clk_out; // divided output
output [1:0] clk_ctl; // divided output for scan freq
input clk; // global clock input
input rst_n; // active low reset


reg clk_out; // clk output (in always block)
reg [1:0] clk_ctl; // clk output (in always block)
reg [14:0] cnt_l; // temp buf of the counter
reg [8:0] cnt_h; // temp buf of the counter
reg [FREQ_DIV_BIT-1:0] cnt_tmp; // input to dff (in always block)

// Combinational logics: increment, neglecting overflow
always @*
    cnt_tmp = {clk_out,cnt_h,clk_ctl,cnt_l} + 1'b1;

// Sequential logics: Flip flops
always @(posedge clk or negedge rst_n)
    if (~rst_n) {clk_out, cnt_h, clk_ctl, cnt_l} <= `FREQ_DIV_BIT'd0;
    else {clk_out,cnt_h, clk_ctl, cnt_l} <= cnt_tmp;

endmodule

```


 


clk_out clk_ctl
MSB 16th-17th

1	9	2	15
---	---	---	----

Modularized Shift Register

Shift Register

  

```


`define BIT_WIDTH 4
module shifter(
  q, // shifter output
  clk, // global clock
  rst_n // active low reset
);

output [^BIT_WIDTH-1:0] q; // output
input clk; // global clock
input rst_n; // active low reset

reg [^BIT_WIDTH-1:0] q; // output

// Sequential logics: Flip flops
always @(posedge clk or negedge rst_n)
  if (~rst_n)
    begin
      q<=`BIT_WIDTH'b0001;
    end
    else
    begin
      q[0]<=q[3];
      q[1]<=q[0];
      q[2]<=q[1];
      q[3]<=q[2];
    end
endmodule
  
```

shifter.v

 

Top Module (shift_reg.v)

```
`define BIT_WIDTH 4
module shift_reg(
    q, // LED output
    clk, // global clock
    rst_n // active low reset
);

output [`BIT_WIDTH-1:0] q; // LED output
input clk; // global clock
input rst_n; // active low reset

wire clk_d; // divided clock
wire [`BIT_WIDTH-1:0] q; // LED output
```

1

```
// Insert frequency divider (freq_div.v)
freqdiv U_FD(
    .clk_out(clk_d), // divided clock output
    .clk(clk), // clock from the crystal
    .rst_n(rst_n) // active low reset
);

// Insert shifter (shifter.v)
shifter U_D(
    .q(q), // shifter output
    .clk(clk_d), // clock from the frequency divider
    .rst_n(rst_n) // active low reset
);

endmodule
```

2

shift_reg.xdc

```

# Clock
set_property PACKAGE_PIN W5 [get_ports {clk}]
set_property IOSTANDARD LVCMOS33 [get_ports {clk}]

# active low reset
set_property PACKAGE_PIN V17 [get_ports {rst_n}]
set_property IOSTANDARD LVCMOS33 [get_ports {rst_n}]

# LEDs
set_property PACKAGE_PIN U16 [get_ports {q[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {q[0]}]
set_property PACKAGE_PIN E19 [get_ports {q[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {q[1]}]
set_property PACKAGE_PIN U19 [get_ports {q[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {q[2]}]
set_property PACKAGE_PIN V19 [get_ports {q[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {q[3]}]
  
```